
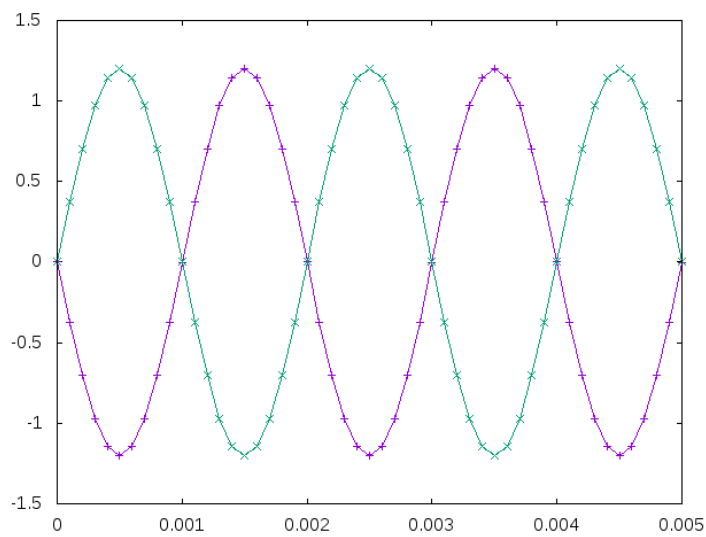


OpAmp-InvertingAmp

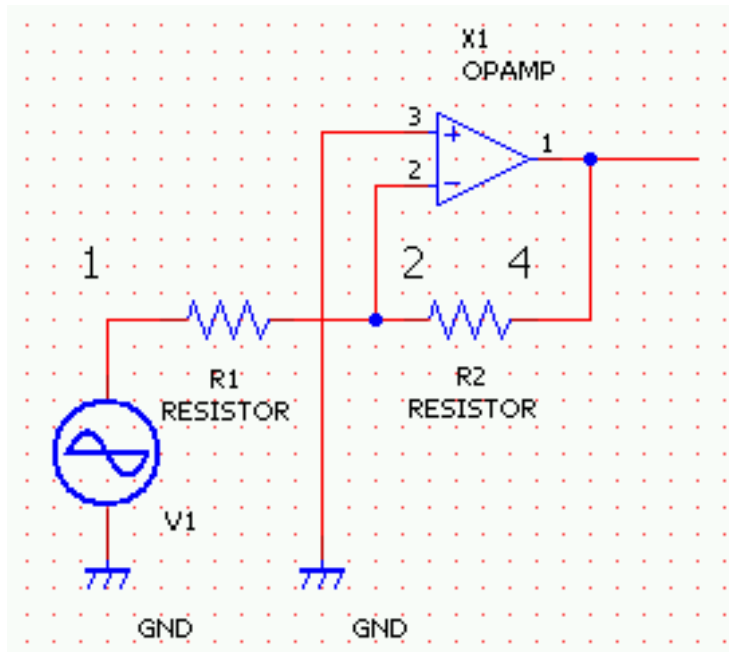

```

*OPAMP INVERTING AMP
V1 1 0 0      sin( 0 1.2 500 )
R1 1 2 100
R2 2 4 100
X1 0 2 4      OPAMP
.SUBCKT OPAMP 1 2 6
R_in 1 2 10MEG
E_gain 3 0 1 2 100k
    
```

```
R_p1    3 4    1k
C_p1    4 0    1.59p
E_buffer    5 0 4 0 1
R_out   5 6    10
.ENDS
.PLOT TRAN v(4) v(1)
.TRAN   .1m 5m 0
.END
.
```

1

¹<http://spice-online.blogspot.com/search/label/OpAmp-InvertingAmp>